

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.1 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.1 and plot the response including the time interval just prior to switch action.

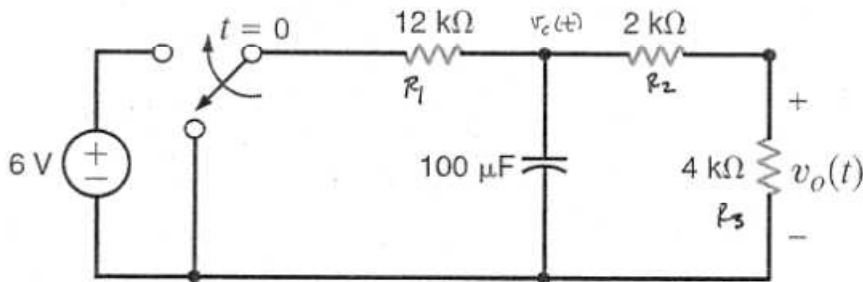


Figure P7.1

SOLUTION:

$$v_c(0^-) = 0V \quad \text{for } t > 0: \quad \frac{6 - v_c}{R_1} + \frac{v_o - v_c}{R_2} - C \frac{dv_c}{dt} = 0 \quad v_o = v_c \frac{R_3}{R_2 + R_3} = \alpha v_c$$

$$\text{Multiply by } \alpha \Rightarrow \frac{6\alpha}{R_1} + \frac{v_o}{R_2} [\alpha - 1] - \frac{v_o}{R_1} - C \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} + v_o \left[\frac{1}{R_1 C} + \frac{1 - \alpha}{R_2 C} \right] - \frac{6\alpha}{R_1 C} = 0 \quad \text{let } \frac{1}{R_1 C} + \frac{1 - \alpha}{R_2 C} = B$$

$$\text{Assume } v_o(t) = K_1 + K_2 e^{-t/\tau} \quad \left\{ \begin{array}{l} \tau = 1/B = C \left[\frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} \right] \\ K_1 = \frac{6\alpha}{R_1 B C} = \frac{6R_3}{R_1 + R_2 + R_3} \end{array} \right.$$


$$\tau = 0.4s \quad K_1 = 1.33V$$

$$v_o(0) = v_c(0) \alpha = 0 = K_1 + K_2 \Rightarrow K_2 = -1.33V$$

$$v_o(t) = 1.33 - 1.33 e^{-2.5t} V$$

$$t = 0^+, \quad v_c(0^+) = 0 \quad v_o(0^+) = \frac{6R_3}{R_1 + R_2 + R_3} = 1.33V$$

$$t = 0^-, \quad v_o(t) = 0$$

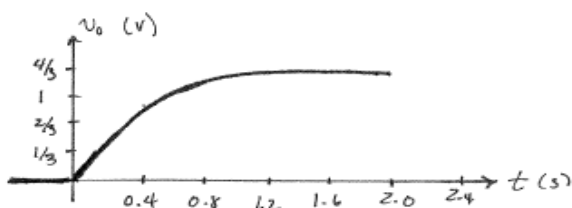

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.2 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.2 and plot the response including the time interval just prior to closing the switch.

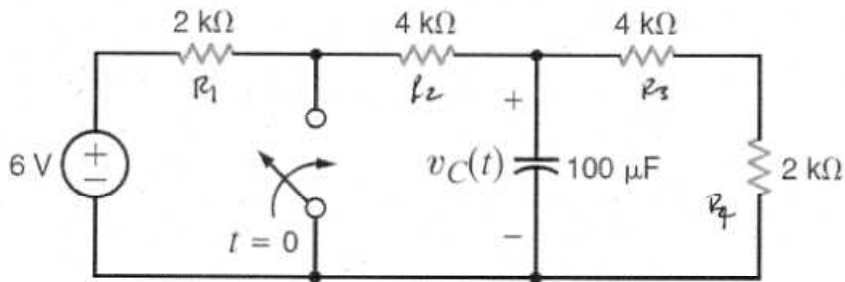


Figure P7.2

SOLUTION: $v_C(t=0^+) = v_C(t=0^-) = \frac{6(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4} = 3V$

for $t > 0$: $\frac{v_C}{R_2} + \frac{v_C}{R_3 + R_4} + C \frac{dv_C}{dt} = 0$ let $v_C(t) = k_1 + k_2 e^{-t/\tau}$


$$k_1 \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right) + k_2 \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right) e^{-t/\tau} - \frac{k_2 C}{\tau} e^{-t/\tau} = 0$$

yields $k_1 = 0$ $\tau = C \left\{ \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4} \right\} = 0.24s$

$v_C(t=0^+) = 3 = k_1 + k_2 \rightarrow k_2 = 3V$

$$v_C(t) = 3e^{-t/0.24} \text{ V}$$

for $t < 0^-$: $v_C(t=0^-) = 3V$

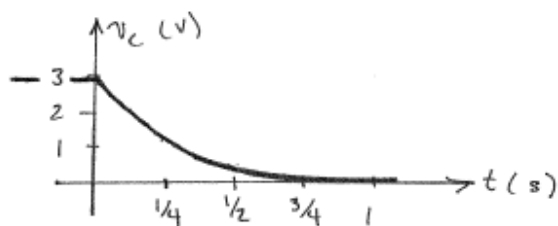

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.5 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.5 and plot the response including the time interval just prior to opening the switch. **CS**

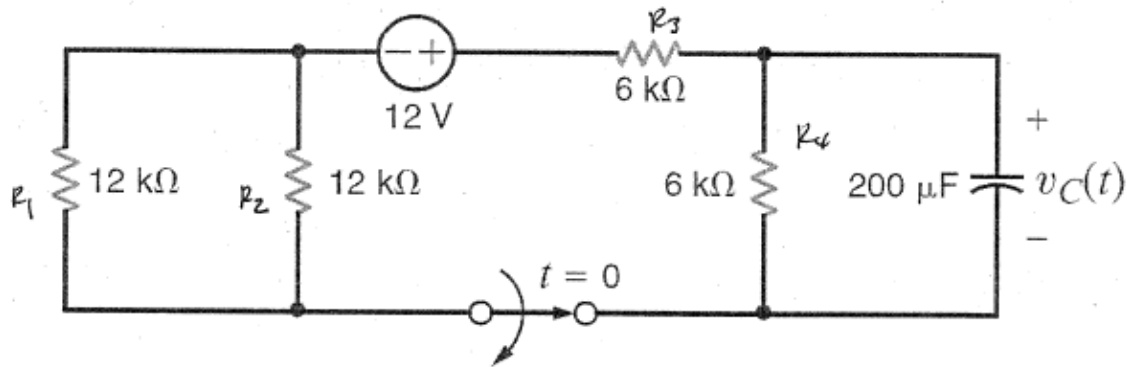


Figure P7.5


SOLUTION: $v_C(t=0^-) = v_C(t=0^+) = \frac{12 R_4}{R_3 + R_4 + R_A}$ $R_A = R_1 // R_2 = 6k\Omega$ $v_C(t=0^+) = 4V$

for $t > 0$; $\frac{v_C}{R_4} + C \frac{dv_C}{dt} = 0 \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{\tau} = 0$

$v_C(t) = K_1 + K_2 e^{-t/\tau} \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{\tau} = 0$

$\tau = R_4 C$ $K_1 = 0$ $v_C(t=0^+) = 4 = K_1 + K_2 \Rightarrow K_2 = 4V$

$$v_C(t) = 4e^{-t/1.2} V$$

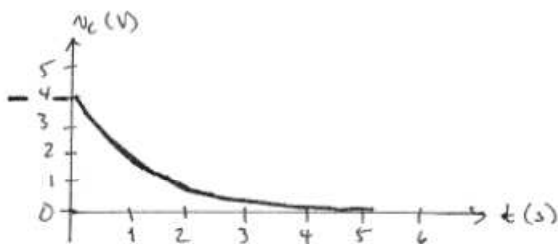

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.7 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.7 and plot the response including the time interval just prior to closing the switch.

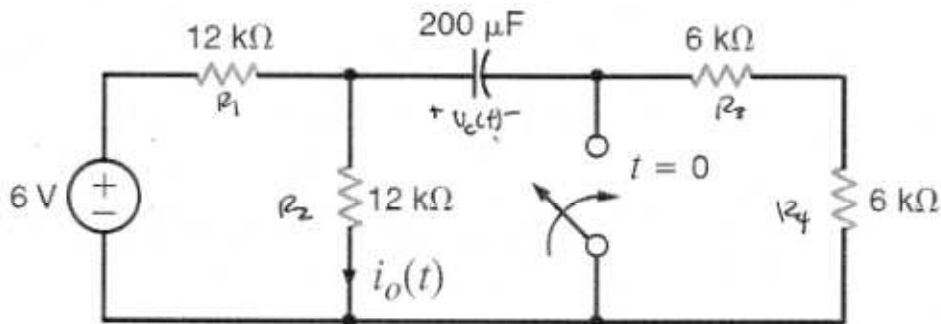


Figure P7.7

SOLUTION: $v_c(0^-) = v_c(0^+) = \frac{6 R_2}{R_1 + R_2} = 3V$ $i_o(t) = \frac{v_c(t)}{R_2}$ for $t > 0$.

for $t > 0$: $\frac{6 - v_c}{R_1} = \frac{v_c}{R_2} + C \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} + v_c \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 C} = 0$

convert to i_o : $\frac{di_o}{dt} + i_o \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 R_2 C} = 0$


$i_o(t) = k_1 + k_2 e^{-t/\tau} \Rightarrow -\frac{k_2}{\tau} e^{-t/\tau} + (k_1 + k_2 e^{-t/\tau}) \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 R_2 C} = 0$

yields $\tau = C \frac{R_1 R_2}{R_1 + R_2} = 1.25$ $k_1 = \frac{6}{R_1 + R_2} = 0.25 \text{ mA}$

$i_o(0^+) = k_1 + k_2 = v_c(0^+) / R_2 = 0.25 \text{ mA} \Rightarrow k_2 = 0$

$i_o(t) = 0.25 \text{ mA}$

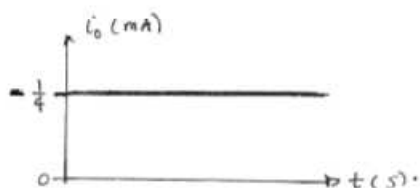$t=0^-$: $v_c(0^-) = 3V$ $i_c(0^-) = 0$ $i_o(0^-) = \frac{6}{R_1 + R_2} = 0.25 \text{ mA}$



نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.10 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.10 and plot the response including the time interval just prior to opening the switch. **CS**


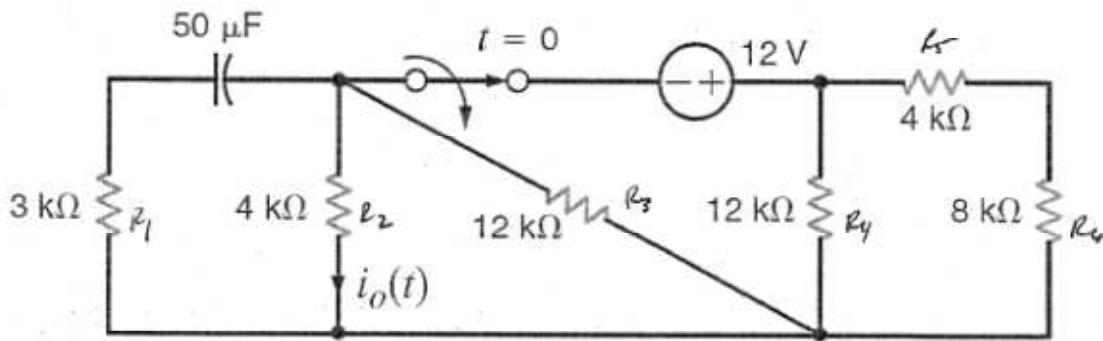


Figure P7.10

SOLUTION:

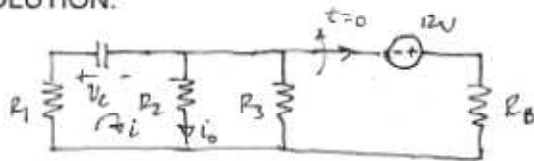

$$R_B = R_4 \parallel (R_5 + R_6) = 6 \text{ k}\Omega$$

$$R_A = R_2 \parallel R_3 = 3 \text{ k}\Omega$$

$$v_c(0^+) = v_c(0^-) = \frac{12 \text{ V}}{R_A + R_B} = 4 \text{ V}$$

$$i_o(0^-) = \frac{-v_c(0^-)}{R_2} = -1 \text{ mA} \quad \checkmark$$

$$\text{For } t > 0, \quad v_c + i R_A + i R_1 = 0 \quad \& \quad i = C \frac{dv_c}{dt} \quad \& \quad i_o = \frac{R_3}{R_2 + R_3} i = \alpha i$$

$$\text{yields,} \quad \frac{dv_c}{dt} + \frac{v_c}{C(R_1 + R_A)} = 0$$

$$\text{or,} \quad \frac{di_o}{dt} + \frac{i_o}{C(R_1 + R_A)} = 0 \quad \text{where } i_o = K_1 + K_2 e^{-t/\tau}$$


$$\text{yields,} \quad \tau = C[R_1 + R_A] = 0.3 \text{ s} \quad K_1 = 0$$

$$i_o(0^+) = \frac{-v_c(0^+)}{R_1 + R_A} \frac{R_3}{R_3 + R_2} = -0.5 \text{ mA} = K_1 + K_2 \Rightarrow K_2 = -0.5 \text{ mA}$$


$$\boxed{i_o(t) = -0.5 e^{-t/0.3} \text{ mA}}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

$t = 0^-$:

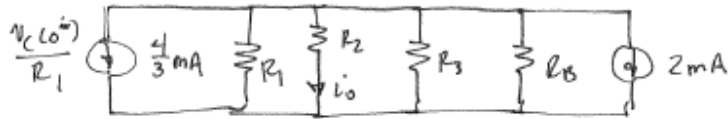
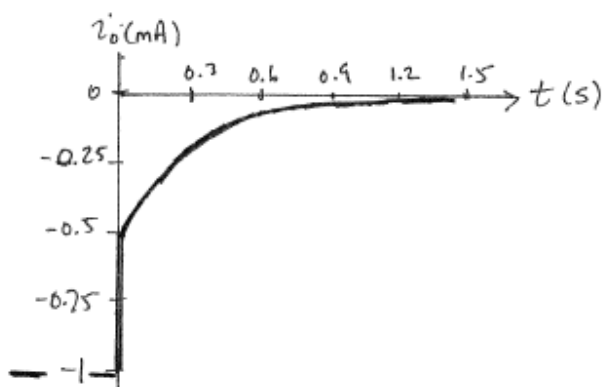
$$i_o(0^-) = - \frac{(2 + 4/3) \times 10^{-3} (1/R_2)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_B}} = -1 \text{ mA}$$



نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.28 Use the step-by-step technique to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.28. CS


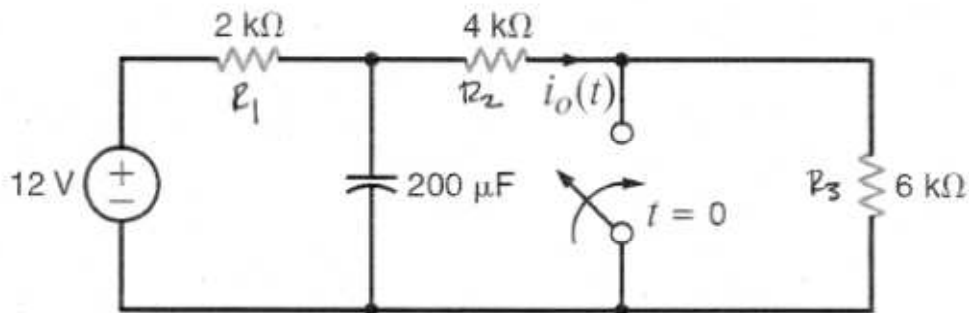



Figure P7.28

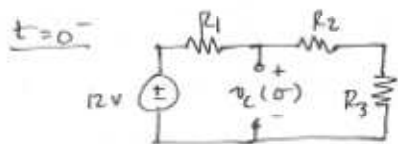SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$




By voltage division: $v_c(0^-) = \frac{12(R_2 + R_1)}{R_1 + R_2 + R_3}$


$v_c(0^-) = 10V$

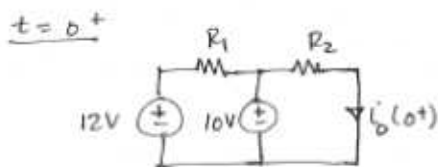

$i_o(0^+) = 10/R_2 = 2.5mA = k_1 + k_2$

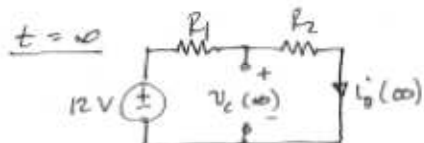

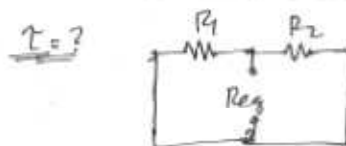$i_o(\infty) = \frac{12}{R_1 + R_2} = 2mA = k_1$



$\tau = LReq$ $Req = R_1 // R_2 = \frac{4}{3} k\Omega$

$\tau = 0.267s$

$i_o(t) = 2 + 0.5e^{-3.75t} \text{ mA}$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.29 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.29.

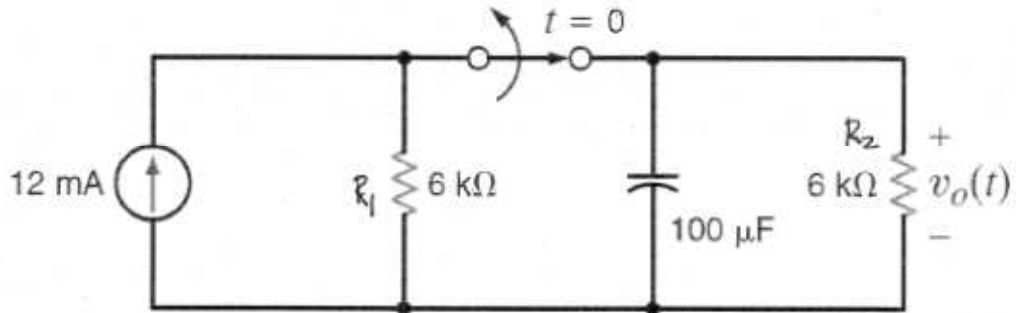


Figure P7.29

SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$

$t = 0^-$

$$v_c(0^-) = 12 \times 10^{-3} \frac{(R_1 R_2)}{R_1 + R_2} = 36 \text{ V}$$

$t = 0^+$

$$v_o(0^+) = 36 = k_1 + k_2$$

$t = \infty$

$$v_o(\infty) = 0 = k_1$$

$\tau = ?$. $\tau = R_{eq} C$ $R_{eq} = R_2 = 6 \text{ k}\Omega$ $\tau = 0.6 \text{ s}$

$$v_o(t) = 36 e^{-t/0.6} \text{ V}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.30 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.30.



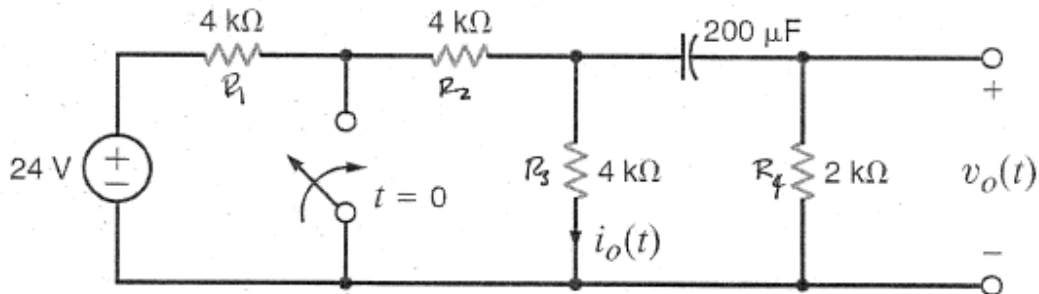


Figure P7.30

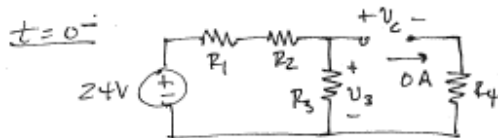SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$



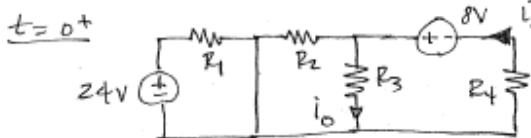
$$v_c = v_3 = \frac{24 R_3}{R_1 + R_2 + R_3} = 8V$$




$$i_s = \frac{8}{R_4 + R_x} \quad R_x = \frac{R_2 R_3}{R_2 + R_3} = 2k\Omega$$
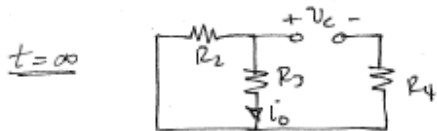
$$i_o = \frac{i_s R_2}{R_2 + R_3} = 1mA = K_1 + K_2$$



$$i_o(\infty) = 0 = K_1$$

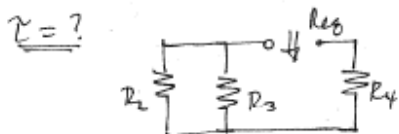

$$\tau = R_{eq} C$$

$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3} + R_4 = 4k\Omega$$

$$\tau = 0.8s$$

$$i_o(t) = e^{-1.25t} \text{ mA}$$


نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.31 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.30 using the step-by-step technique.


SOLUTION:

$$v_o(t) = k_1 + k_2 e^{-t/\tau}$$
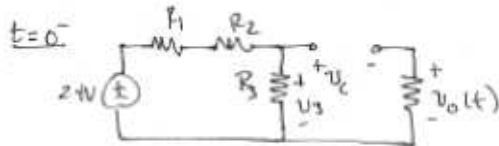
$$R_1 = R_2 = R_3 = 4k\Omega \quad R_4 = 2k\Omega$$



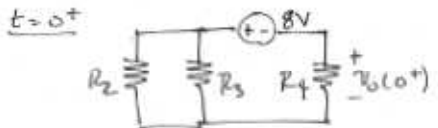
$$v_c = v_3 = \frac{2 + R_3}{R_1 + R_2 + R_3} = 2V$$




$$R_x = R_2 // R_3 = 2k\Omega$$
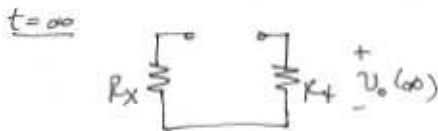
$$v_o(0^+) = -\frac{8R_4}{R_4 + R_x} = -4V = k_1 + k_2$$



$$v_o(\infty) = 0 = k_1$$

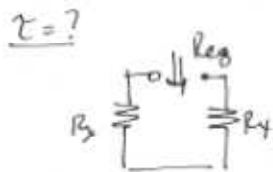

$$\tau = R_{eq} C \quad R_g = R_x + R_4 = 4k\Omega$$

$$\tau = 0.8s$$

$$v_o(t) = -4e^{-1.25t} \text{ V}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.33 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.33 using the step-by-step method. CS


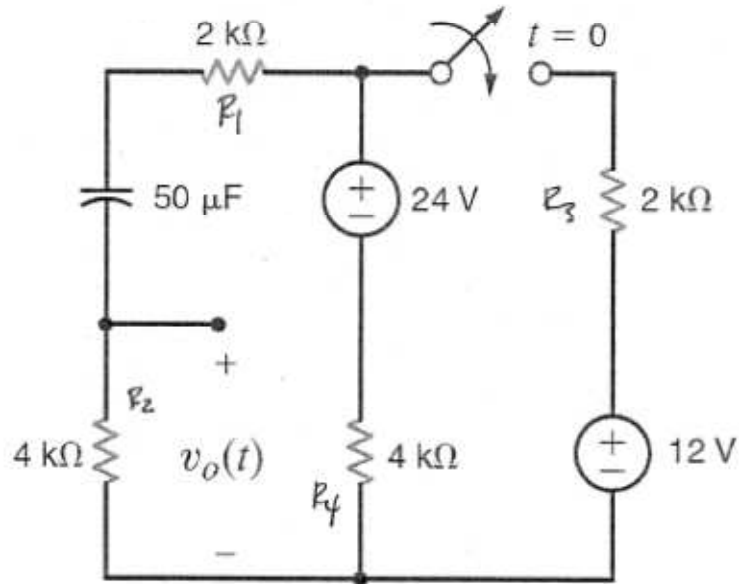



Figure P7.33

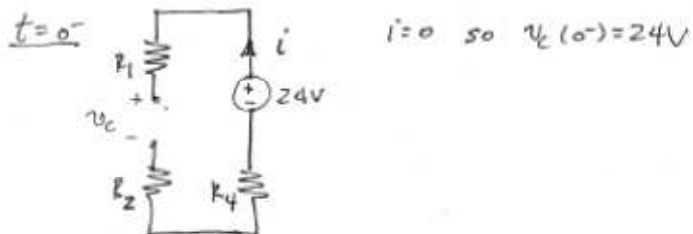SOLUTION: $v_o(t) = K_1 + K_2 e^{-t/\tau}$



نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

$t=0^+$

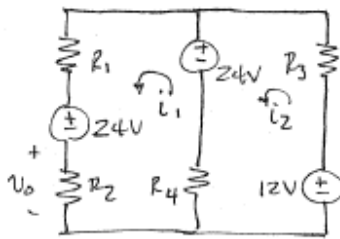

$$24 = i_1 (R_1 + R_2 + R_4) - i_2 R_4 + 24$$

$$\text{or, } i_1 (R_1 + R_2 + R_4) = i_2 R_4$$


$$12 = i_2 (R_3 + R_4) + 24 - i_1 R_4$$

$$\text{or } i_1 R_4 - i_2 (R_3 + R_4) = 12$$

$$i_1 = -\frac{12}{11} \text{ mA} \quad v_o(0^+) = i_1 R_2$$


$$v_o(0^+) = \frac{48}{11} \text{ V} = k_1 + k_2$$

$t=\infty$

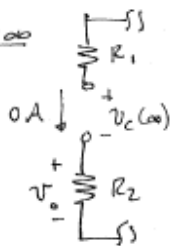

$$v_o(\infty) = 0 = k_1$$

$t=?$

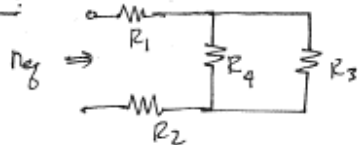

$$R_{eq} = R_1 + R_2 + \frac{R_3 R_4}{R_3 + R_4} = 7.33 \text{ k}\Omega$$

$$\tau = 367 \text{ ms}$$

$$v_o(t) = -4.36 e^{-2.73t} \text{ V}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.34 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.34 using the step-by-step method. **PSV**



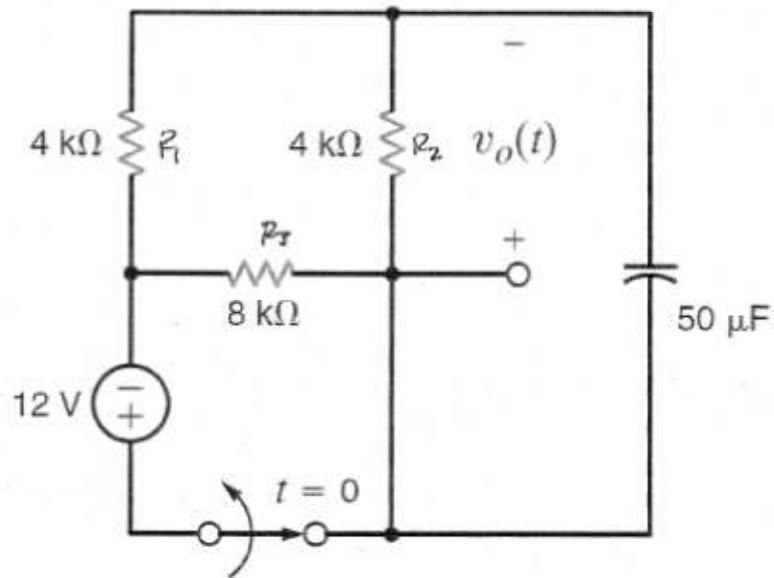


Figure P7.34

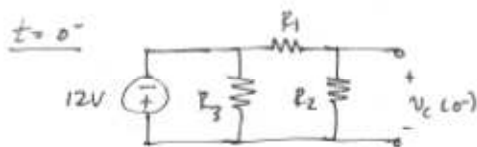SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$



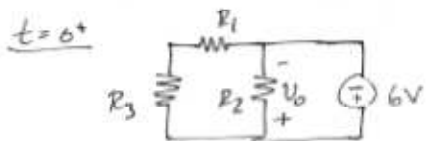
$$v_c(0^-) = -12 \left(\frac{R_2}{R_1 + R_2} \right) = -6V$$



$$v_o(0^+) = 6V = k_1 + k_2$$

$t = \infty$

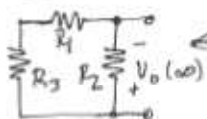

$$v_o(\infty) = 0 = k_1 \quad R_{eq} = R_2 (R_1 + R_3) / (R_1 + R_2 + R_3) = 3k\Omega$$

$$\tau = R_{eq} C = 150ns$$

$$v_o(t) = 6e^{-6.67t} V$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.37 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.37 using the step-by-step method. CS


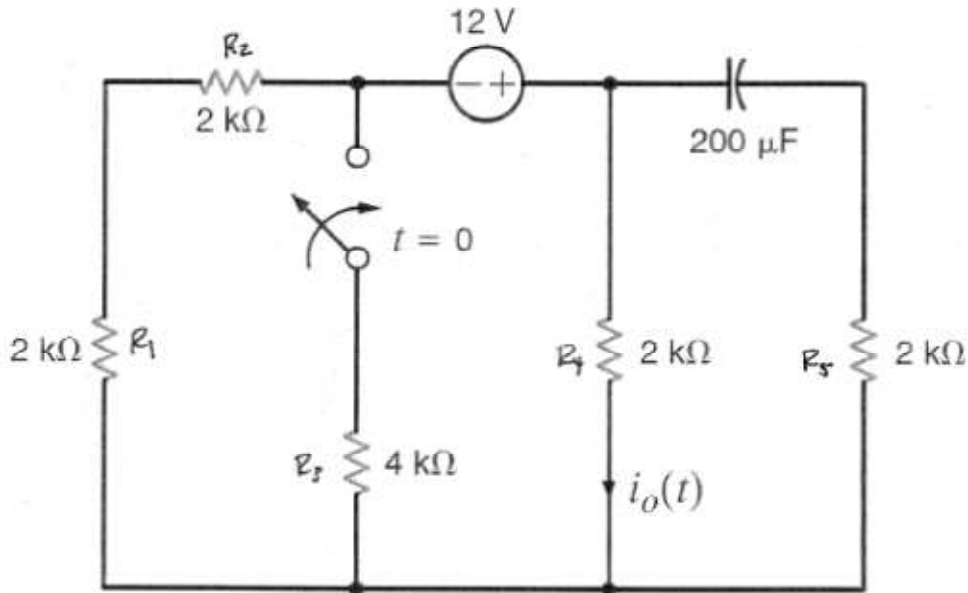
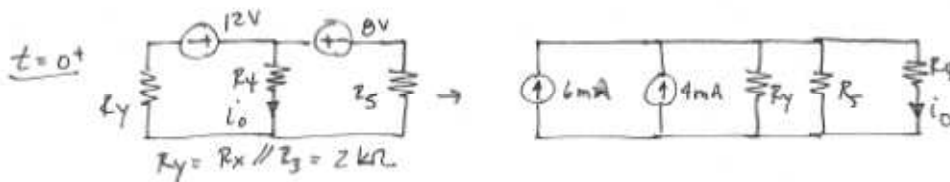


Figure P7.37


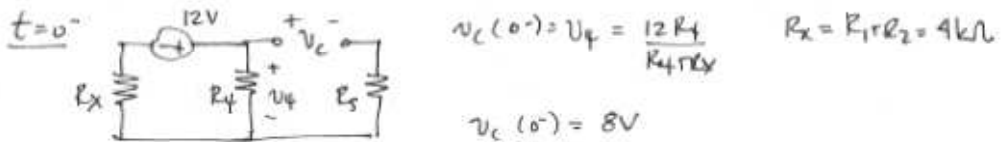
SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$



$i_o(0^+) = \frac{10^{-2} R_2}{R_2 + R_4} = 3.33 \text{ mA} = K_1 + K_2$

$R_2 = R_y \parallel R_5 = 1 \text{ k}\Omega$

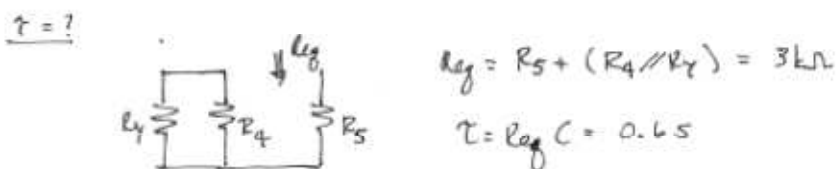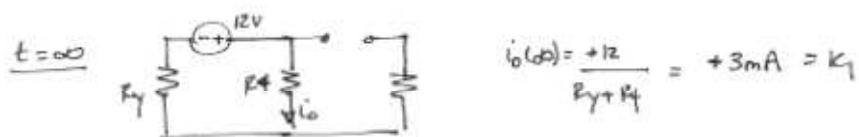نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول



$$i_o(t) = 3 + 0.33 e^{-1.67t} \text{ mA}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.38 Use the step-by-step technique to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.38.


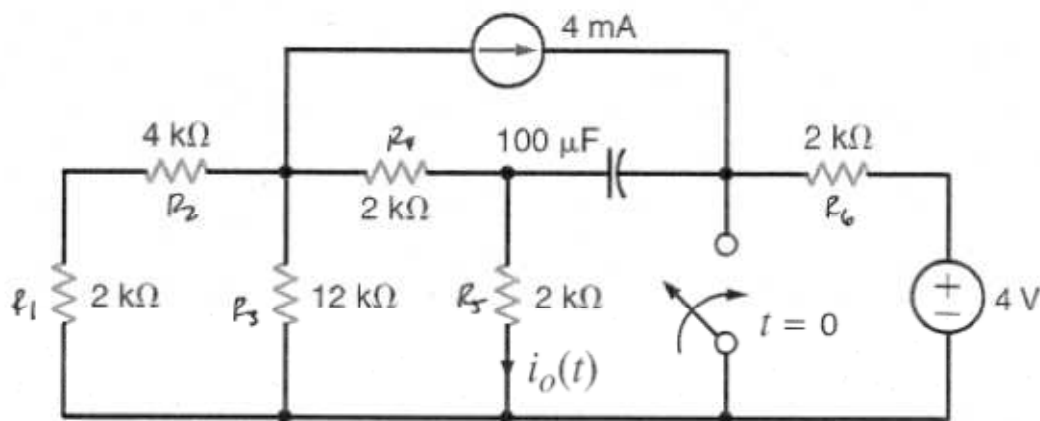


Figure P7.38

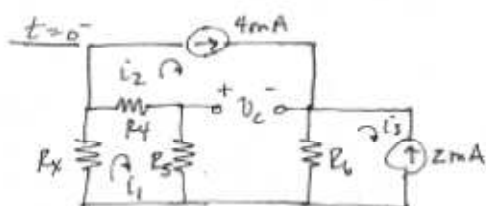SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$




$$R_x = R_3 \parallel (R_1 + R_2) = 4 \text{ k}\Omega$$

$$i_2 = 4 \text{ mA} \quad i_3 = -2 \text{ mA}$$

$$i_1(R_x + R_4 + R_5) - i_2(R_4 + R_5) = 0$$


$$i_1 = 2 \text{ mA}$$
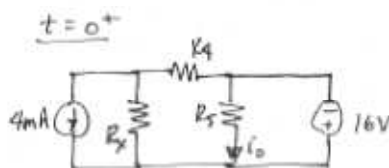
$$v_L(0^-) = (i_1 - i_2)R_5 + (i_3 - i_2)R_6 = -16 \text{ V}$$



$$i_o(0^+) = \frac{-16}{R_5} = -8 \text{ mA}$$

$$K_1 + K_2 = -8 \text{ mA}$$

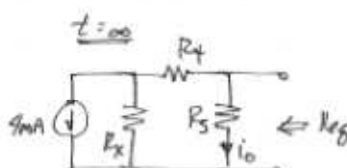

$$i_o(\infty) = \frac{-4 \times 10^{-3} R_x}{R_x + R_4 + R_5}$$

$$i_o(\infty) = -2 \text{ mA} = K_1$$

$\tau = ?$

$$R_{eq} = R_5 \parallel (R_4 + R_6) = 1.5 \text{ k}\Omega$$

$$\tau = R_{eq} C = 0.15 \text{ s}$$

$$i_o(t) = -2 - 6e^{-6.67t} \text{ mA}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.19 In the network in Fig. 7.19, find $i_o(t)$ for $t > 0$ using the differential equation approach. CS

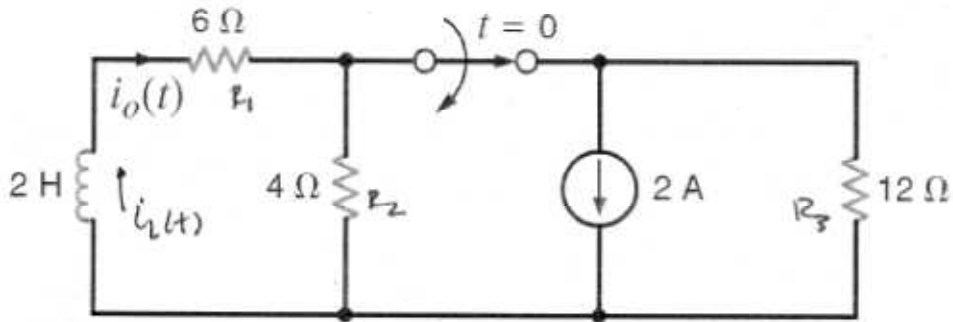


Figure P7.19

SOLUTION: $t=0^-: i_L(0^-) = \frac{2 \left(\frac{1}{R_1} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{2}{3} \text{ A}$


$t=0^+ \quad i_o = i_L = \frac{2}{3} \text{ A}$

$t > 0 \quad L \frac{di_L}{dt} + i_o (R_1 + R_2) = 0 \quad \& \quad i_L = i_o \Rightarrow \frac{di_o}{dt} + \frac{(R_1 + R_2)}{L} i_o = 0$

$i_o = k_1 + k_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_1 + R_2} = \frac{1}{5} \text{ s} \quad k_1 = 0$

$k_2 = i_o(0^+) - k_1 = \frac{2}{3} \text{ A}$

$i_o(t) = 0.67 e^{-5t} \text{ A}$

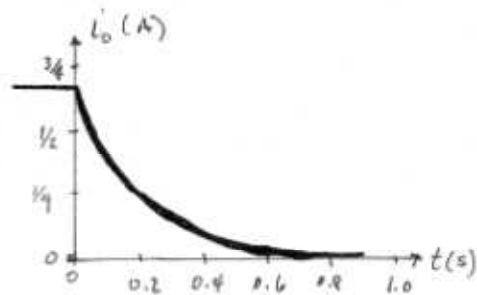

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.20 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.20 and plot the response including the time interval just prior to switch movement. **PSV**

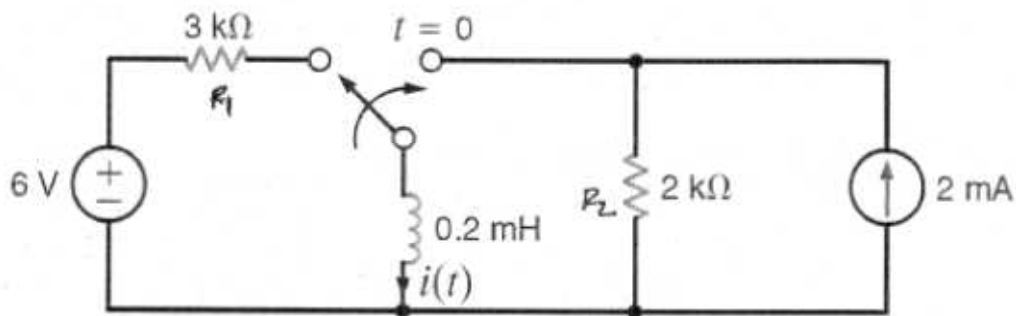


Figure P7.20

SOLUTION:

$$t = 0^- : i(0^-) = \frac{6}{R_1} = 2 \text{ mA} = i(0^+)$$

$$t = 0^+ : i(0^+) = 2 \text{ mA}$$



$$t > 0 : 4 = R_2 i + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R_2}{L} i - \frac{4}{L} = 0 \quad i = K_1 + K_2 e^{-t/\tau}$$

$$\tau = L/R_2 = 0.1 \mu\text{s} \quad K_1 = 4/R_2 = 2 \text{ mA}$$

$$K_2 = i(0^+) - K_1 = 0$$

$$i(t) = 2 \text{ mA}$$

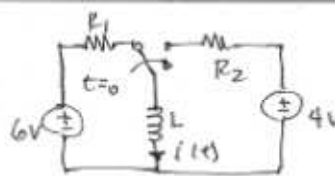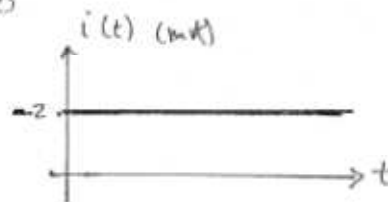

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.22 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.22 and plot the response including the time interval just prior to opening the switch.


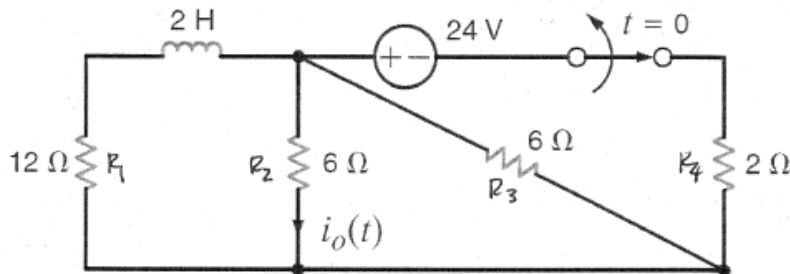


Figure P7.22

SOLUTION:

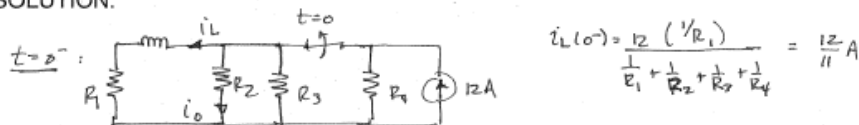

$$i_L(0^-) = 12 \left(\frac{1/R_1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right) = \frac{12}{11} \text{ A}$$

$$i_o(0^-) = \frac{12 \text{ A} \left(\frac{1/R_2}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{24}{11} \text{ A}$$


$$t = 0^+ \quad i_L(0^+) = \frac{12}{11} \text{ A} \quad i_o(0^+) = -\frac{i_L(0^+) R_3}{R_2 + R_3} = -\frac{6}{11} \text{ A}$$

$$t > 0: \quad L \frac{di_L}{dt} + i_L (R_1 + R_2) = 0 \quad R_B = R_2 // R_3 \quad i_o = -\frac{i_L R_3}{R_2 + R_3}$$

$$\frac{di_o}{dt} + \left(\frac{R_1 + R_2}{L} \right) i_o = 0 \quad \text{and} \quad i_o(t) = K_1 + K_2 e^{-t/\tau}$$

$$\tau = \frac{L}{R_1 + R_2} = \frac{2}{15} \text{ s} \quad K_1 = 0 \quad K_2 = i_o(0^+) - K_1 = -\frac{6}{11} \text{ A}$$

$$i_o(t) = -0.545 e^{-7.5t} \text{ A}$$

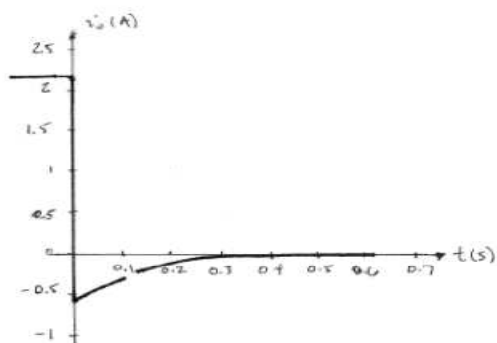

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.25 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.25 and plot the response including the time interval just prior to opening the switch.

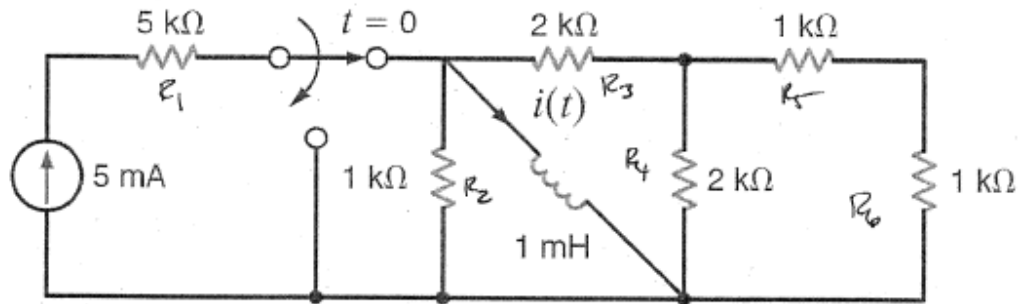



Figure P7.25

SOLUTION:

$$t=0^-: i(0^-) = 5 \text{ mA}$$

$$t=0^+: i(0^+) = i(0^-) = 5 \text{ mA}$$

$t > 0$:

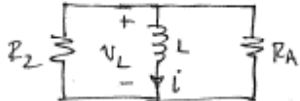

$$R_A = R_3 + \left\{ R_4 \parallel [R_5 + R_6] \right\}$$

$$R_A = 3 \text{ k}\Omega$$

$$\tau = \frac{L(R_A + R_2)}{R_A R_2} = \frac{1}{3} \mu\text{s}$$


$$i(t) = 5 e^{-2.5 \times 10^5 t} \text{ mA}$$

$$i + \frac{v_L}{R_2} + \frac{v_L}{R_A} = 0 \quad \& \quad v_L = L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R_A R_2}{(R_A + R_2)L} i = 0$$

$$i = K_1 + K_2 e^{-t/\tau}$$
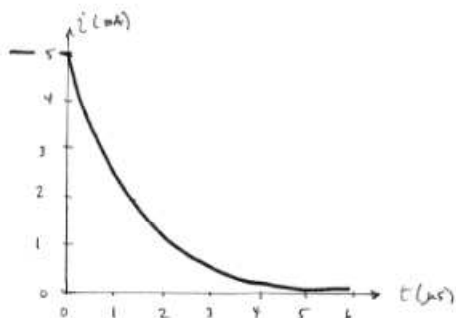
$$K_1 = 0 \quad K_2 = i(0^+) - K_1 = 5 \text{ mA}$$



نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.39 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.39.



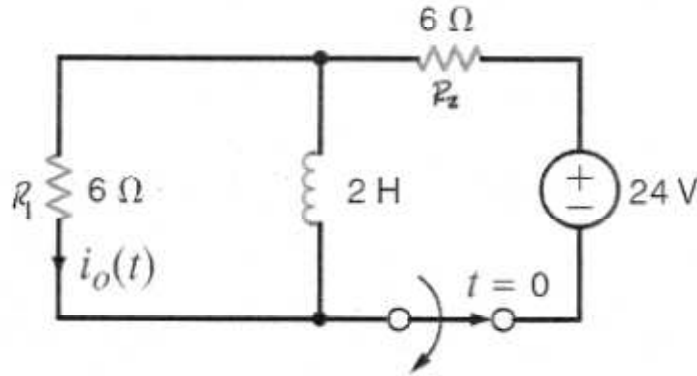


Figure P7.39

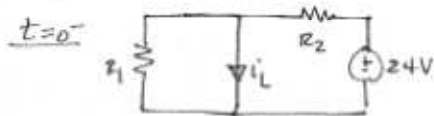SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$




$$i_L(0^-) = 24/R_2 = 4 \text{ A}$$

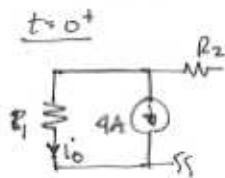


$$i_o(0^+) = -4 \text{ A}$$

$$k_1 + k_2 = -4 \text{ A}$$

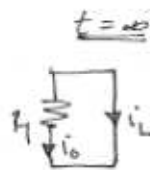

$$i_o(\infty) = 0 = k_1$$

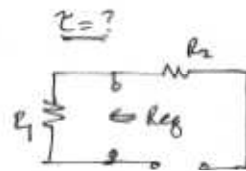

$$R_{eq} = R_1 = 6 \Omega$$

$$\tau = L/R_{eq} = \frac{1}{3} \text{ s}$$

$$i_o(t) = -4e^{-3t} \text{ A}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.41 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.41 using the step-by-step method. CS


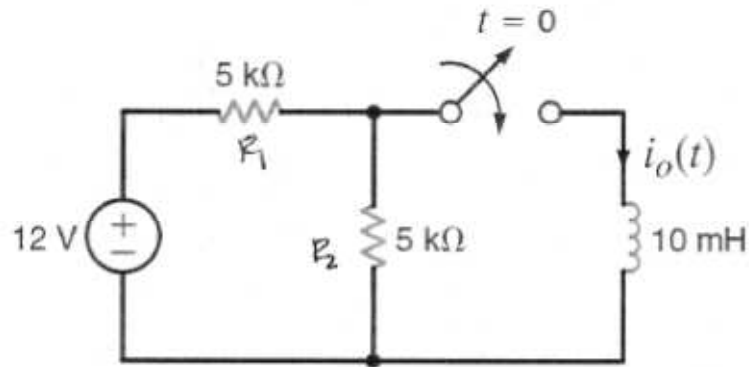



Figure P7.41

SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$

$t=0^-$

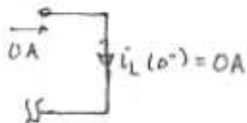


$t=0^+$

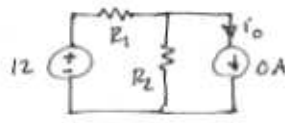


$$i_o(0^+) = 0 = k_1 + k_2$$

$t=\infty$

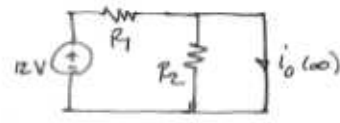

$$i_o(\infty) = \frac{12}{R_1} = 2.4 \text{ mA} = k_1$$

$\tau = ?$

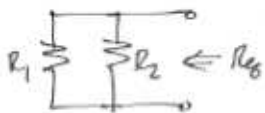

$$R_{eq} = R_1 // R_2 = 2.5 \text{ k}\Omega$$

$$\tau = \frac{L}{R_{eq}} = 4 \mu\text{s}$$

$$i_o(t) = 2.4 - 2.4 e^{-2.5 \times 10^5 t} \text{ mA}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.42 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.42 using the step-by-step method.


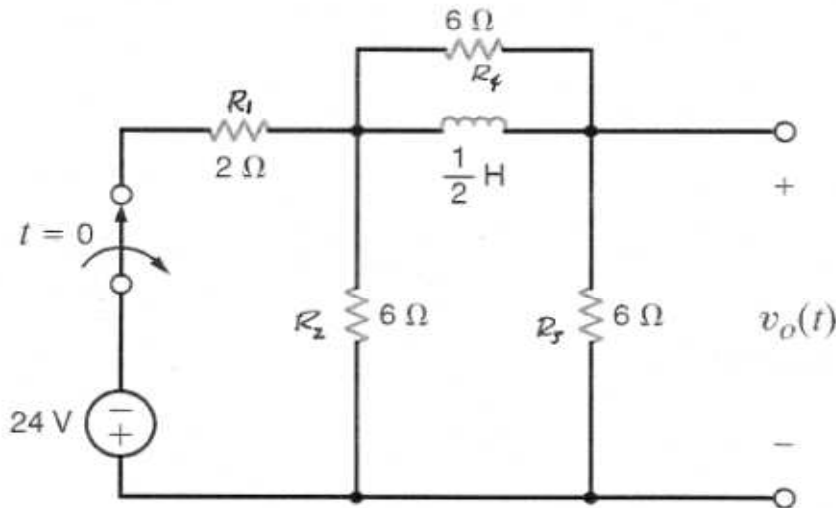
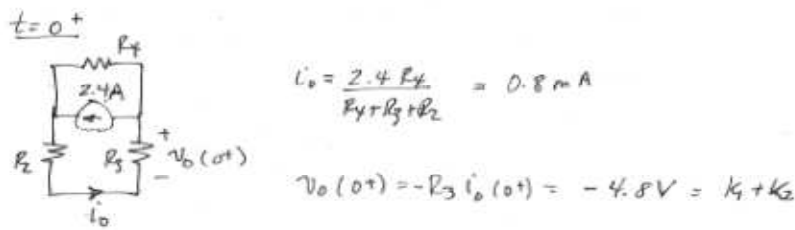



Figure P7.42

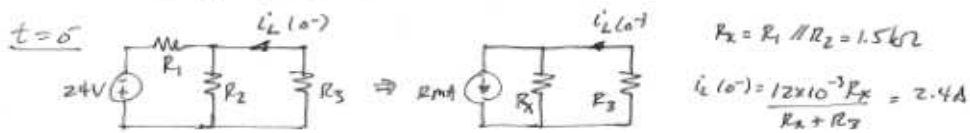SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$




نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

$t = \infty$

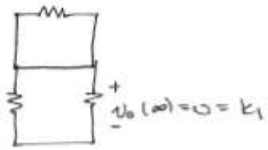

$\tau = ?$

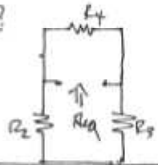

$$R_{eq} = R_1 // (R_2 + R_3) = 4 \Omega$$

$$\tau = L / R_{eq} = \frac{1}{8} \text{ s}$$

$$v_o(t) = -4.8e^{-8t} \text{ V}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.43 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.43. **PSV**



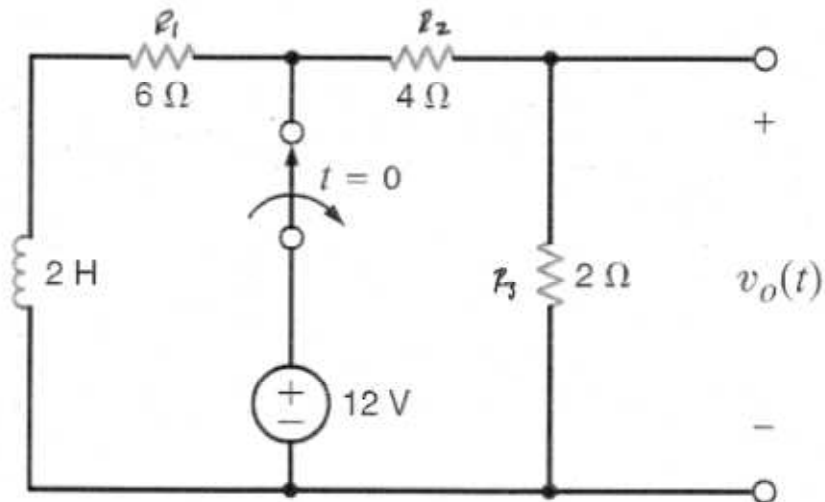


Figure P7.43

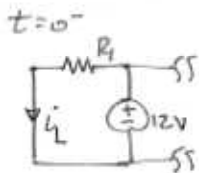
SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$



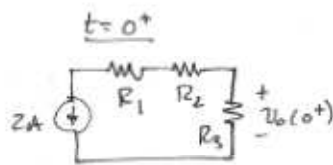
$$i_L(0^-) = \frac{12}{R_1} = 2 \text{ A}$$


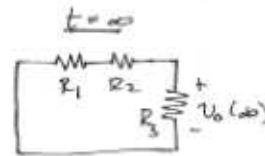
$$v_o(0^+) = -2R_3 = -4 \text{ V} = k_1 + k_2$$



$$v_o(\infty) = 0 = k_1$$

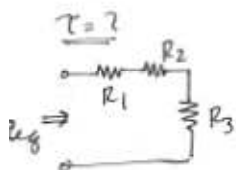

$$\tau = L/R_{eq} = \frac{1}{6} \text{ s}$$

$$v_o = -4e^{-6t} \text{ V}$$

$$R_{eq} = R_1 + R_2 + R_3 = 12 \Omega$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.48 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.48 using the step-by-step technique.


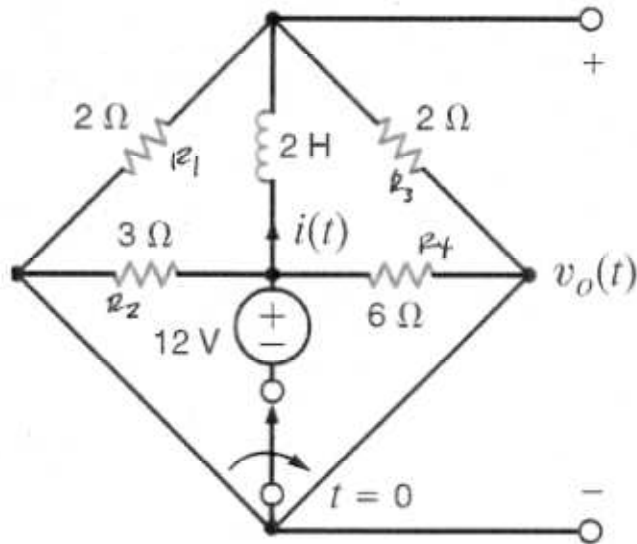


Figure P7.48

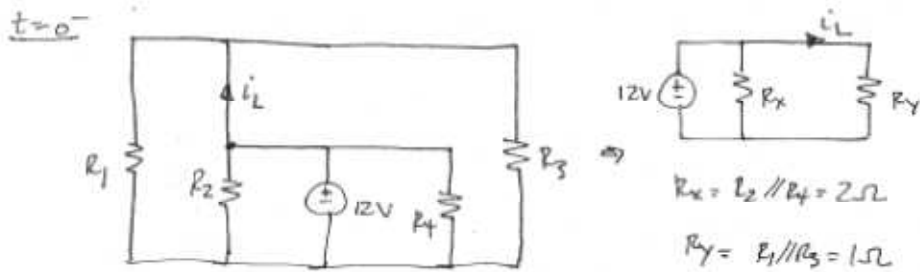SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$




$$i_L = \frac{12}{R_y} = 12 \text{ A}$$


$$R_x = R_2 // R_4 = 2 \Omega$$

$$R_y = R_1 // R_3 = 1 \Omega$$

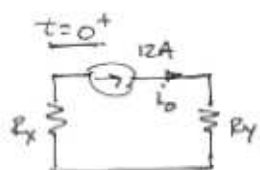
نمونه مسائل حل شده از مبحث مدارهای مرتبه اول



$$i_0 = 12A = k_1 + k_2$$

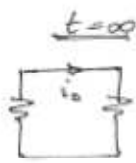

$$i_0 = 0 = k_1$$

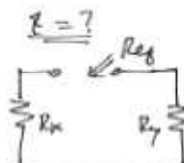

$$R_{eq} = R_1 + R_2$$

$$R_{eq} = 3\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{3} S$$

$$i_0 = 12e^{-1.5t} A$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.49 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.49.


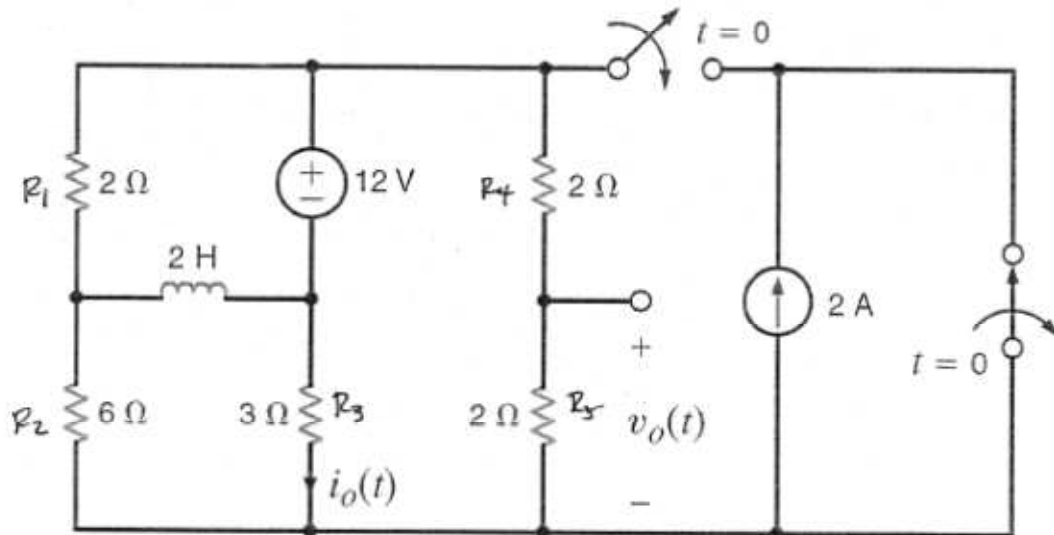


Figure P7.49

SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$

$t=0^-$

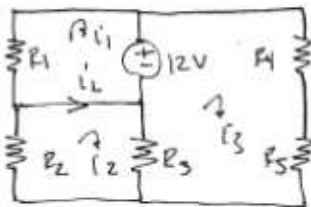

$$i_L(t=0^-) = i_2 - i_1 = \frac{20}{3}\text{ A}$$

mesh analysis:

$$i_1 R_1 + 12 = 0 \Rightarrow i_1 = -6\text{ A}$$


$$i_2 (R_2 + R_3) - i_3 R_3 = 0 \Rightarrow i_3 = 3i_2$$

$$12 = i_3 (R_3 + R_4 + R_5) - i_2 R_3 \Rightarrow 7i_3 - 3i_2 = 12$$

$$\text{yields } i_3 = 2\text{ A} \text{ \& } i_2 = \frac{2}{3}\text{ A}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

$t=0^+$

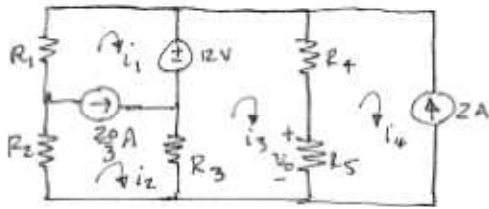

$$v_0 = R_5 (i_3 - i_4) = 5.41 \text{ V}$$

$$5.41 = K_1 + K_2$$

$$i_2 - i_1 = 20/3$$


$$i_4 = -2$$

$$12 = i_3 (R_4 + R_5) - i_2 R_3 - i_4 (R_4 + R_5)$$

$$0 = i_1 R_1 + i_2 R_2 + i_3 (R_4 + R_5) - i_4 (R_4 + R_5)$$

$$i_3 = 0.706 \text{ A}$$

$t=\infty$

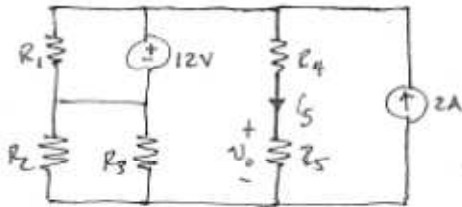


$$v_0(\infty) = i_5 R_5 = 2 i_5$$

Find i_5 by superposition:
$$i_5 = \frac{12}{R_x + R_y} + \frac{2 R_x}{R_x + R_y} = \frac{8}{3} \text{ A}$$

$$v_0 = \frac{16}{3} = 5.33 \text{ V} = K_1$$

$\tau = ?$

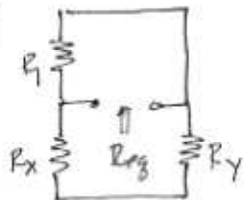

$$R_{\text{eq}} = R_1 \parallel (R_x + R_y) = 1.5 \Omega$$

$$\tau = L / R_{\text{eq}} = \frac{4}{3} \text{ s}$$

$$v_0 = 5.33 + 0.08 e^{-0.75t} \text{ V}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.59 Find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.59 using the step-by-step method.


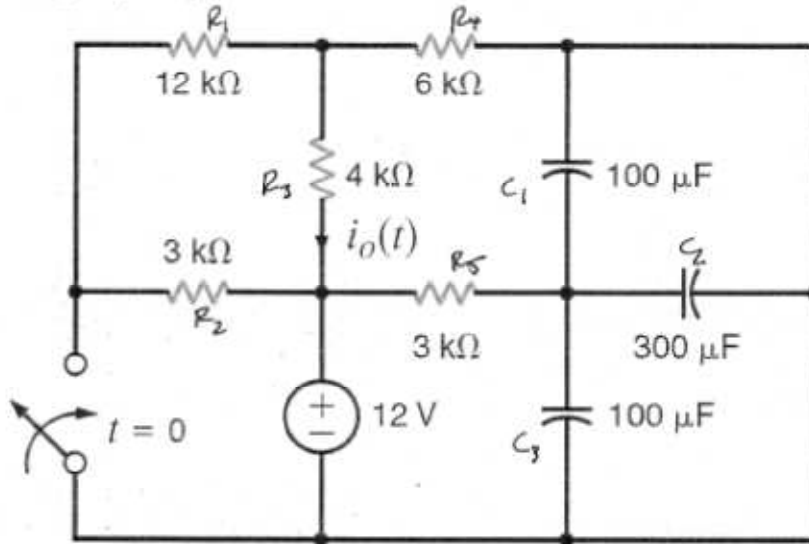


Figure P7.59


SOLUTION:

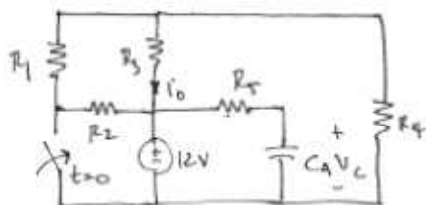


$$C_A = C_1 + C_2 + C_3 = 500 \mu\text{F}$$

$$t = 0^-: v_C = 12\text{V}$$

$$t = 0^+: v_C = 12\text{V}$$

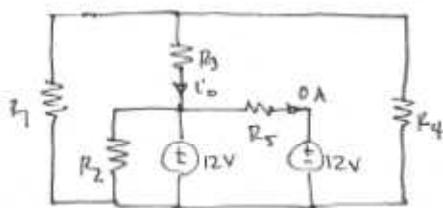

⇒

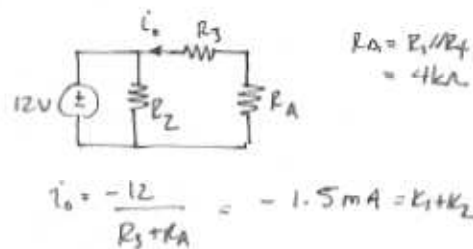

$$R_A = R_4 \parallel R_5 = 4\text{k}\Omega$$

$$i_o = \frac{-12}{R_3 + R_A} = -1.5\text{mA} = k_1 + k_2$$

$t = \infty$ Same situation as $t = 0^+$, $i_o = -1.5\text{mA} = k_1 \Rightarrow k_2 = 0$

$$i_o(t) = -1.5\text{mA}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.60 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.60 using the step-by-step method.


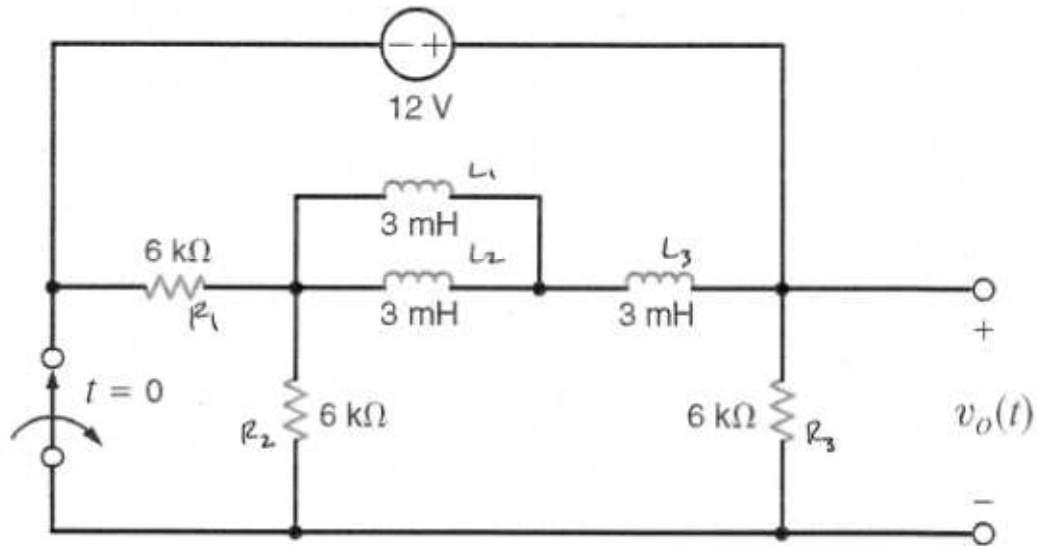



Figure P7.60

SOLUTION:

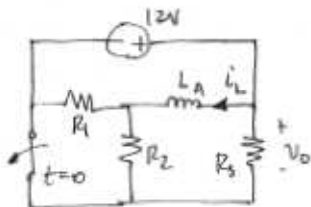

$$L_A = L_3 + \frac{L_1 L_2}{L_1 + L_2} = 4.5 \text{ mH}$$
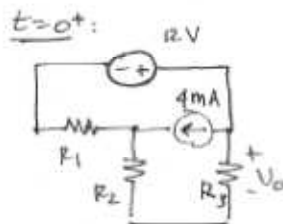
$$t=0^- \quad i_L = \frac{12}{R_1} + \frac{12}{R_2} = 4 \text{ mA}$$




$$\text{Superposition: } v_o = \frac{12 R_3}{R_1 + R_2 + R_3} - \frac{4 \times 10^{-3} R_1 R_3}{R_1 + R_2 + R_3}$$

$$v_o(0^+) = 4 \text{ V} = k_1 + k_2$$


نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

$t = \infty$:

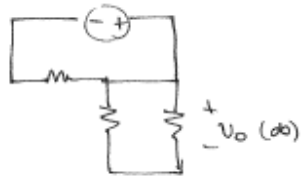

$$v_o(\infty) = 0 \text{ V} = k_1$$

$\tau = ?$

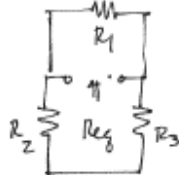


$$R_{eq} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} = 4 \text{ k}\Omega \quad \tau = \frac{L}{R_{eq}} = 1.125 \mu\text{s}$$


$$v_o(t) = -4 e^{-8.88 \times 10^5 t} \text{ V}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

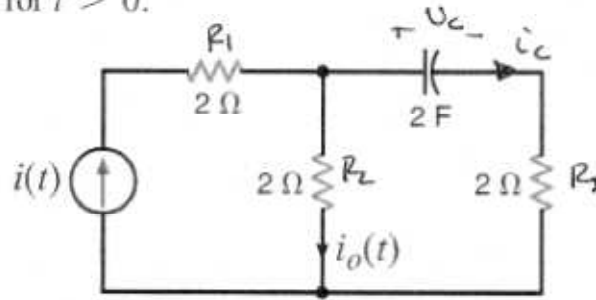7.62 The current source in the network in Fig. P7.62a is defined in Fig. P7.62b. The initial voltage across the capacitor must be zero. (Why?) Determine the current $i_o(t)$ for $t > 0$.



(a)

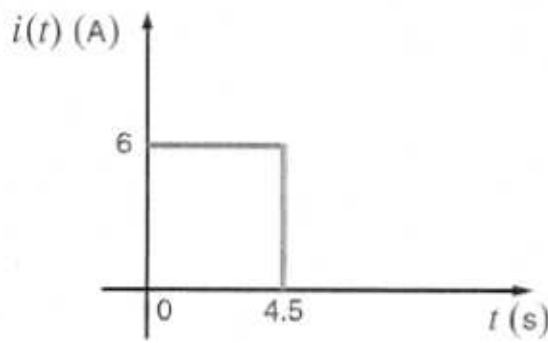

(b)

Figure P7.62

SOLUTION:

Since $i(t)$ is 0 for $t < 0$, no charge has accumulated on the capacitor and v_c must be 0.

$$t = 0^- : v_c = 0$$

$$t = 0^+ : v_c = 0, \quad i_o = \frac{i R_3}{R_2 + R_3} = 3 \text{ A} = k_1 + k_2$$

$$v_c(t) = k_3 + k_4 e^{-t/\tau}$$

$$i_o(t) = k_1 + k_2 e^{-t/\tau}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

$$t \rightarrow \infty \quad i_c = 0 \text{ A} \quad i_o = 6 = k_1 \quad v_c = i_o R_2 = 12 \text{ V} = k_3$$


$$k_2 = -3 \text{ A} \quad k_4 = -12 \text{ V}$$

$$\tau = C R_{eq} = C (R_2 + k_3) = 8 \text{ s}$$

$$\left. \begin{aligned} i_o(t) &= 6 - 3e^{-t/8} \text{ A} \\ v_c(t) &= 12 - 12e^{-t/8} \text{ V} \end{aligned} \right\} 0 \leq t \leq 4.5 \text{ s}$$

$$t = 4.5 \text{ s} \quad v_c(4.5) = 5.16 \text{ V} \quad i_o = k_5 + k_6 e^{-t'/8} \quad t > 4.5 \text{ s}$$

$$t' = t - 4.5$$

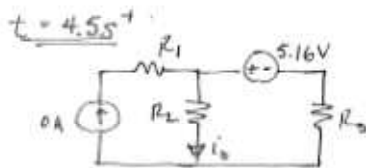

$$i_o = \frac{5.16}{R_2 + k_3} = 1.29 = k_5 + k_6$$

$$t \rightarrow \infty \quad i_o = 0 = k_5 \Rightarrow k_6 = 1.29 \text{ A}$$

$$\tau_2 = C R_{eq2} = C [R_2 + k_3] = 8 \text{ s}$$


$$i_o(t) = 1.29 e^{-t'/8} \text{ A} \quad t > 4.5 \text{ s}$$

Final answer


$$i_o(t) = \begin{cases} 6 - 3e^{-t/8} \text{ A} & 0 \leq t \leq 4.5 \text{ s} \\ 1.29 e^{-(t-4.5)/8} \text{ A} & t > 4.5 \text{ s} \end{cases}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

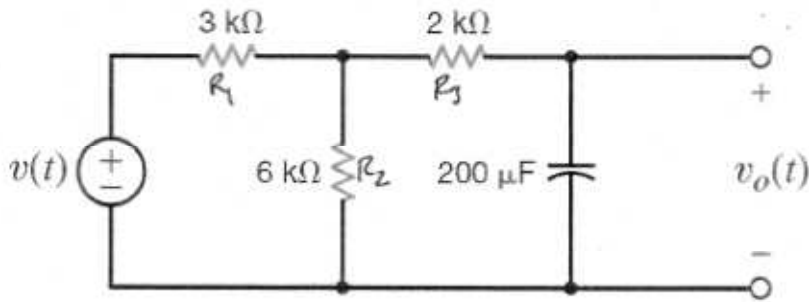7.63 Determine the equation for the voltage $v_o(t)$ for $t > 0$, in Fig. P7.63a when subjected to the input pulse shown in Fig. P7.63b.



(a)

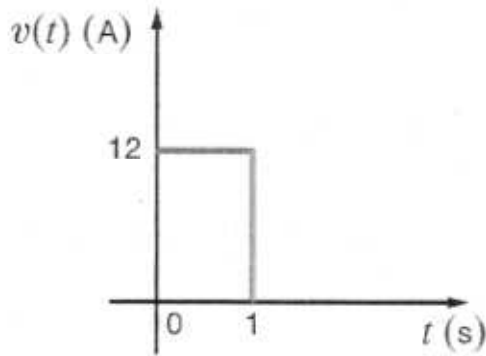


(b)


Figure P7.63

SOLUTION: $v_o = k_1 + k_2 e^{-t/\tau}$

$t = 0^- \quad v_o = 0$

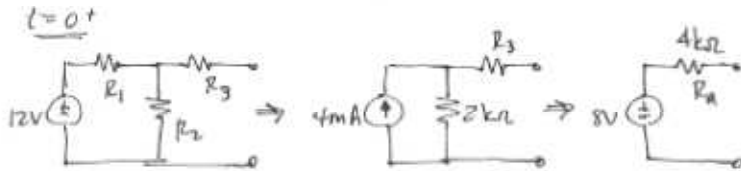

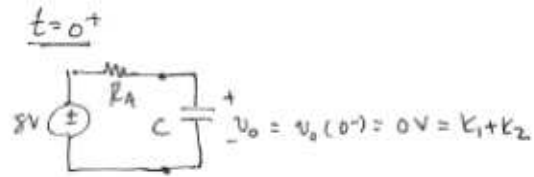نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول



$t=\infty: v_o = 9V = k_1$

$\tau = RC = 0.8s$

$v_o(t) = 9 - 9e^{-1.25t} \text{ V} \quad 0 < t \leq 1$

for $t > 1s$, $v_o = k_3 + k_4 e^{-t'/\tau}$ $t' = t - 1$

at $t=1^-$, $v_o = 5.71V$

at $t=1^+$, $v_o = 5.71V = k_3 + k_4$

at $t=\infty$ $v_o = 0 = k_3 \Rightarrow k_4 = 5.71V$

$$v_o = \begin{cases} 9 - 9e^{-1.25t} \text{ V} & 0 \leq t \leq 1 \\ 5.71 e^{-1.25(t-1)} \text{ V} & t > 1 \end{cases}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.64 Find the output voltage $v_o(t)$ in the network in Fig. P7.64 if the input voltage is $v_i(t) = 5(u(t) - u(t - 0.05))$ V.


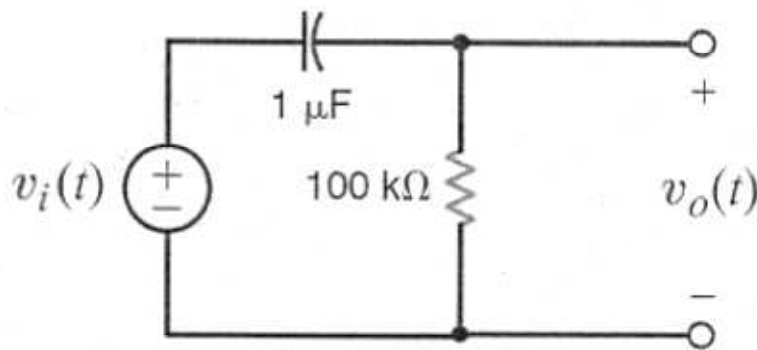


Figure P7.64

SOLUTION:

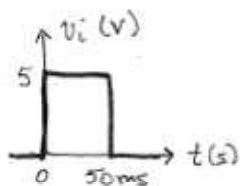

$$\text{For } 0 \leq t \leq 50 \text{ ms} \quad v_o = k_1 + k_2 e^{-t/\tau}$$

$$\text{For } t > 50 \text{ ms} \quad v_o = k_3 + k_4 e^{-t/\tau}$$

$$t = 0^- \quad v_o = 0 \quad \& \quad v_c = 0 \text{ V}$$

$$t = 0^+ \quad v_c = 0 \quad \& \quad v_o = v_i = 5 = k_1 + k_2$$

$$t \rightarrow \infty \quad v_o = 0 = k_1 \Rightarrow k_2 = 5 \text{ V}$$

$$\tau = CR = 0.15 \Rightarrow v_o(t) = 5e^{-10t} \quad 0 \leq t \leq 50 \text{ ms}$$

$$\text{at } t = 50 \text{ ms}^- \quad v_o = 3.03 \text{ V} \quad \& \quad v_c = 1.97 \text{ V}$$

$$t = 50 \text{ ms}^+ \quad v_c = 1.97 \text{ V} \quad \& \quad v_o = v_i - v_c = -1.97 \text{ V} = k_3 + k_4$$

$$t \rightarrow \infty \quad v_o = 0 = k_3 \Rightarrow v_o(t) = -1.97 e^{-10(t-0.05)} \text{ V} \quad t > 50 \text{ ms}$$

$$v_o = \begin{cases} 5e^{-10t} \text{ V} & 0 \leq t \leq 50 \text{ ms} \\ -1.97e^{-10(t-0.05)} \text{ V} & t > 50 \text{ ms} \end{cases}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.65 The voltage $v(t)$ shown in Fig. P7.65a is given by the graph shown in Fig. P7.65b. If $i_L(0) = 0$, answer the following questions: (a) how much energy is stored in the inductor at $t = 3$ s?, (b) how much power is supplied by the source at $t = 4$ s?, (c) what is $i(t = 6$ s)?, and (d) how much power is absorbed by the inductor at $t = 3$ s?

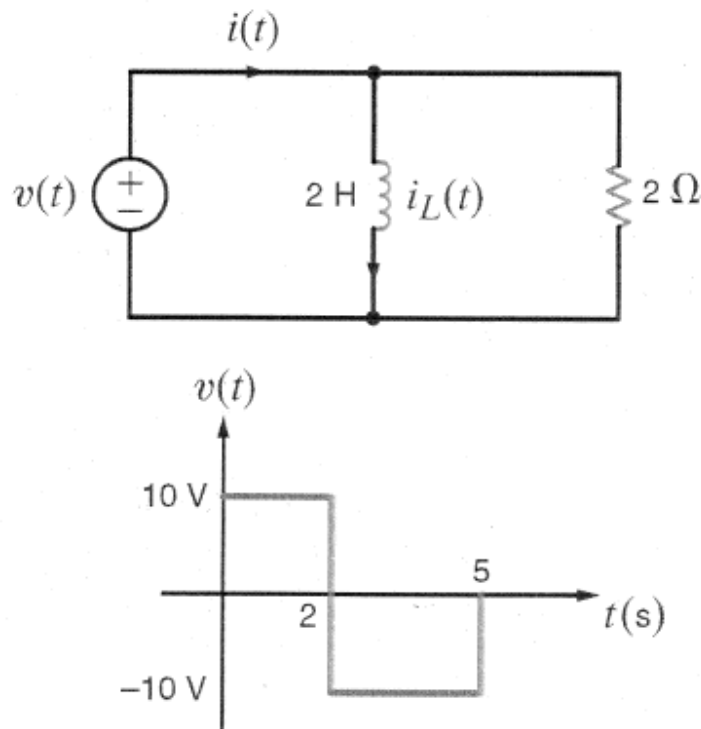


Figure P7.65

SOLUTION:

$$a) \quad w_L = \frac{1}{2} L i_L^2 \quad i_L(t) = \frac{1}{L} \int v_L dt = \frac{1}{L} \int v dt$$

$$i_L(3) = \frac{10}{2} t \Big|_0^2 - \frac{10}{2} t \Big|_2^3 = 5 \text{ A} \quad \boxed{w_L(3) = 25 \text{ J}}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

$$b) p_s(t) = v(t) i(t) = v(t) [i_L(t) + v(t)/R]$$

$$i_L(4) = \frac{1}{L} \int_0^4 v(t) dt = 5t \Big|_0^4 - 5t \Big|_2^4 = 0A$$

$$p_s(4) = v^2(4)/R = 100/2$$

$$p_s(4) = 50W$$

$$c) i'(6) = i_L(6) + \frac{v(6)}{R} \quad v(6) = 0$$

$$i_L(6) = \frac{1}{L} \int_0^6 v(t) dt = 5t \Big|_0^6 - 5t \Big|_2^6 = -5A$$

$$i'(6) = -5A$$

$$d) p_L = v(t) i_L(t) \quad i_L(3) = 5A \quad v(3) = -10V$$

$$p_L(3) = -50W \text{ absorbed}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.66 In the circuit in Fig. P7.66, $v_R(t) = 100e^{-400t}$ V for $t < 0$. Find $v_R(t)$ for $t > 0$.

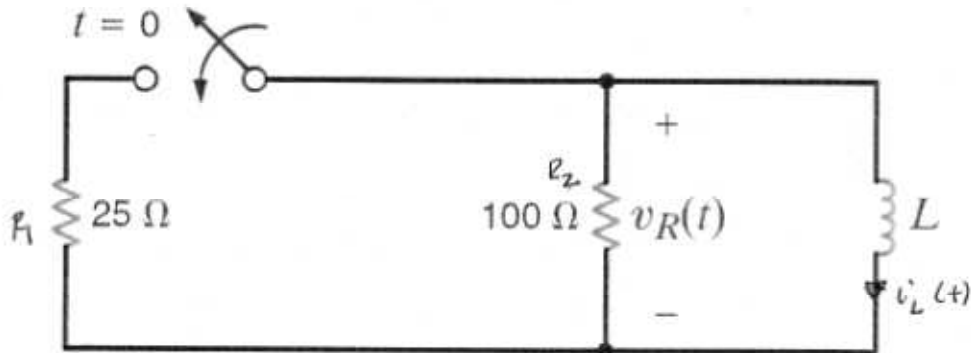


Figure P7.66

SOLUTION:

$$\underline{t=0^-} \quad v_R(0^-) = 100\text{V} \quad i_L(0^-) = -\frac{v_R(0^-)}{R_2} = -1\text{A}$$

$$\tau_1 = \frac{L}{R_2} = \frac{1}{400} \Rightarrow L = \frac{1}{4}\text{H}$$

$$\underline{t=0^+} \quad i_L(0^+) = -1\text{A} \quad v_R(0^+) = -\frac{i_L(0^+) R_2 R_1}{R_1 + R_2} = 20\text{V} = K_1 + K_2$$

$$\underline{t=\infty} \quad v_R = 0 = K_1 \Rightarrow K_2 = 20\text{V}$$

$$\underline{\tau} \quad \tau_2 = \frac{L(R_1 + R_2)}{R_1 R_2} = \frac{1}{20}\text{s}$$

$$\boxed{v_R(t) = 20e^{-20t}\text{V}}$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.67 Given that $v_{C1}(0^-) = -10 \text{ V}$ and $v_{C2}(0^-) = 20 \text{ V}$ in the circuit in Fig. P7.67, find $i(0^+)$.


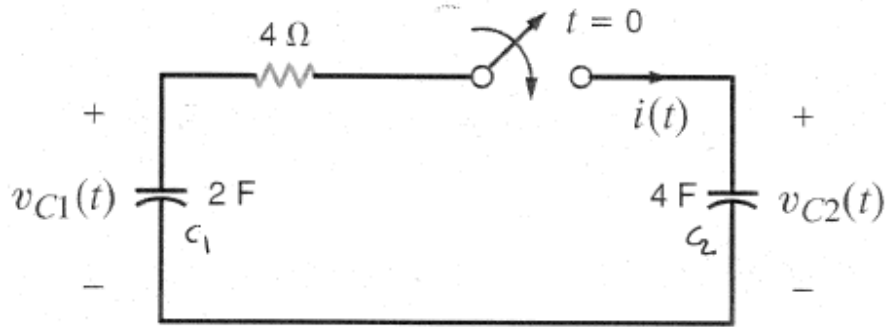


Figure P7.67

SOLUTION:

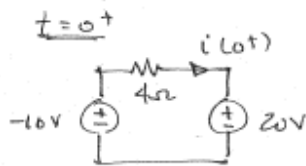v_{C1} & v_{C2} cannot change instantaneously.



$$i(0^+) = \frac{-10 - 20}{4} = -7.5 \text{ A}$$

$$i(0^+) = -7.5 \text{ A}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

7.68 The switch in the circuit in Fig. P7.68 is closed at $t = 0$. If $i_1(0^-) = 2$ A, determine $i_2(0^+)$, $v_R(0^+)$, and $i_1(t = \infty)$.

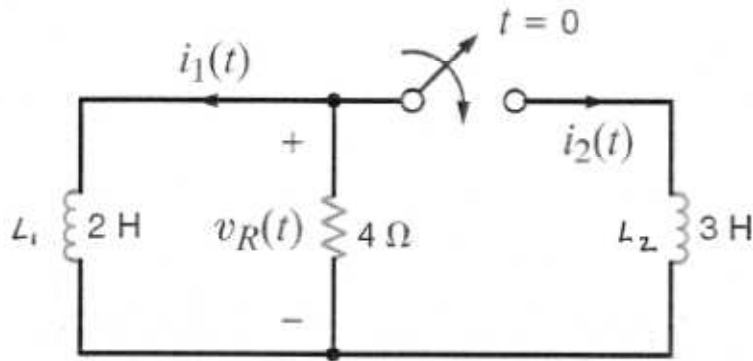


Figure P7.68

SOLUTION:

$$\underline{t=0^-} \quad i_1(0^-) = 2\text{ A} \quad i_2(0^-) = 0\text{ A}$$

$$\underline{t=0^+} \quad i_1(0^+) = i_1(0^-) = 2\text{ A} \quad i_2(0^+) = i_2(0^-) = 0\text{ A}$$

$$v_R(0^+) = -i_1(0^+) (4) = -8\text{ V}$$

$v_R(0^+) = -8\text{ V}$ $i_2(0^+) = 0\text{ A}$ $i_1(\infty) = 0\text{ A}$

$$\underline{t=\infty} \quad \text{all } v(t) \text{ \& } i(t) \rightarrow 0$$

$$i_1(\infty) = 0$$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.69 In the network in Fig. P7.69 find $i(t)$ for $t > 0$. If $v_{C1}(0^-) = -10$ V, calculate $v_{C2}(0^-)$.


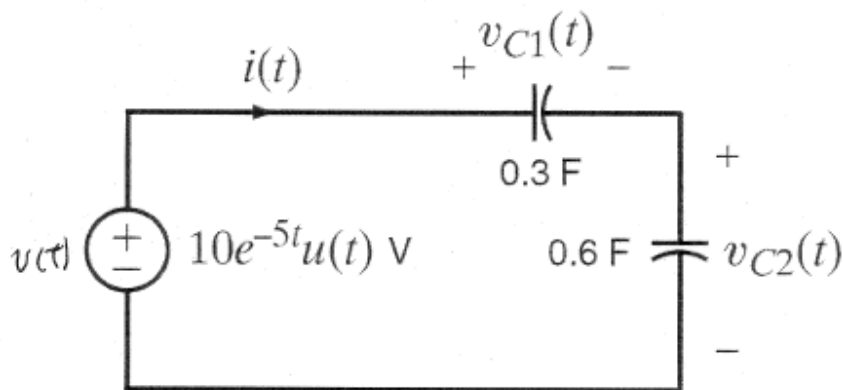
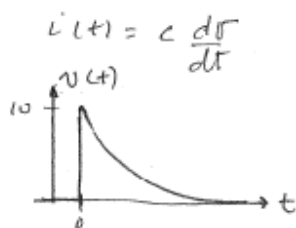
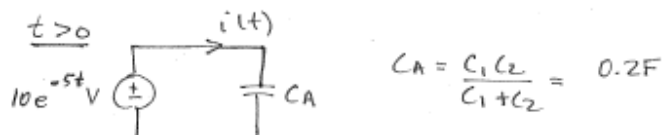


Figure P7.69

SOLUTION:

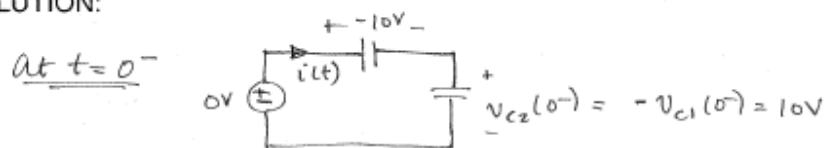

$$\frac{dv}{dt} = 10\delta(t) - 50e^{-5t} \quad t \geq 0$$

$$i(t) = 2\delta(t) - 10e^{-5t} \text{ A} \quad t \geq 0$$

$$v_{C2}(0^-) = 10 \text{ V}$$

نمونه مسائل حل شده از مبحث مدارهای مرتبه اول

- 7.71 Given that $i(t) = 13.33e^{-t} - 8.33e^{-0.5t}$ A for $t > 0$ in the network in Fig. P7.71, find the following: (a) $v_C(0)$, (b) $v_C(t = 1 \text{ s})$, and (c) the capacitance C .

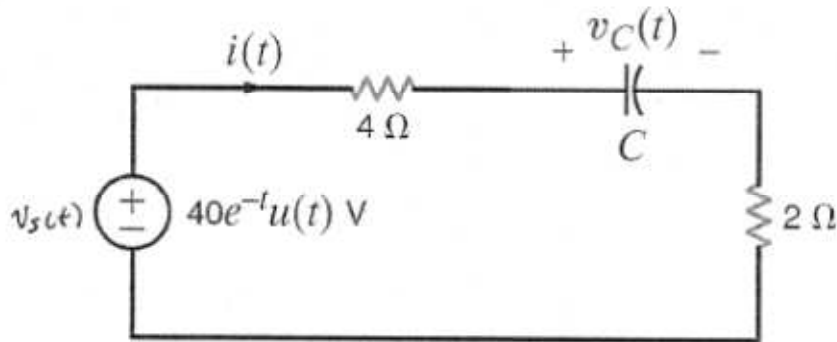


Figure P7.71

SOLUTION:

a) $v_C(0^-) = v_s(0^-) = 0 \text{ V} = v_C(0^+)$ $v_C(0) = 0 \text{ V}$

b) $v_C(t) = \frac{1}{C} \int i \, dt + K$
 $= \frac{1}{C} [16.66e^{-t/2} - 13.33e^{-t}] + K$

$v_C(0) = 0 = \frac{1}{C} [3.33] + K \Rightarrow K = -3.33/C$

Need C .

c) $\tau = 2 = C[1+2] = 6C \Rightarrow \boxed{C = 1/3 \text{ F}}$

Back to b)

$K = -10$ $v_C(t) = 50e^{-t/2} - 40e^{-t} - 10$

$v_C(1) = 5.61 \text{ V}$

نمونه مسائلی حل شده از مبحث مدارهای مرتبه اول

7.72 Given that $i(t) = 2.5 + 1.5e^{-4t}$ A for $t > 0$ in the circuit in Fig. P7.72, find R_1 , R_2 , and L .

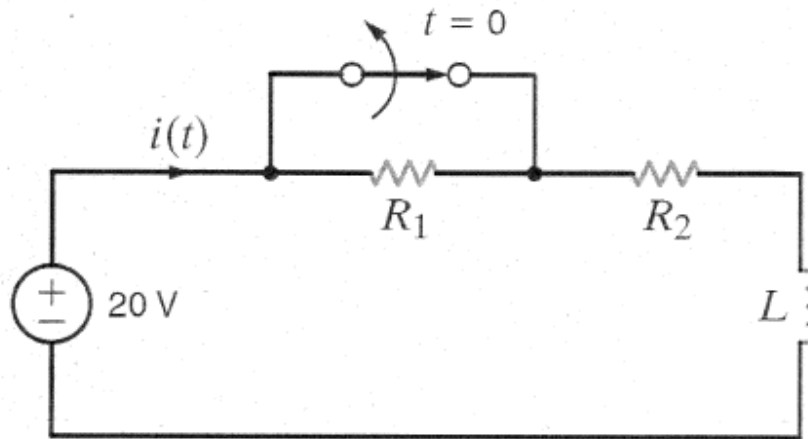


Figure P7.72

SOLUTION:

$$i(t) = 2.5 + 1.5e^{-4t} = k_1 + k_2 e^{-t/\tau}$$

$$k_1 = 2.5 = i(\infty) = \frac{20}{R_1 + R_2} \Rightarrow R_1 + R_2 = 8 \Omega$$

$$k_1 + k_2 = 4 = i(0^+) = i_L(0^+) = i_L(0^-) = \frac{20}{R_2} \Rightarrow R_2 = 5 \Omega$$

$$R_1 = 3 \Omega$$

$$\tau = \frac{1}{4} = \frac{L}{R_1 + R_2} \quad L = 2H$$

$L = 2H$ $R_1 = 3 \Omega$ $R_2 = 5 \Omega$
--